

Icom IC-765 Notes

Don Stalkowski, VE3HUR

September 10, 2002

Version 1.02

Contents

1	Introduction	3
1.1	Warnings	3
2	General Information	4
2.1	Description	4
2.2	Relation to the IC-761	5
2.3	Filters	6
2.4	Power Supply	6
2.5	Trimmer Capacitors	6
2.6	Serial Numbers and Dates	6
2.7	Icom Email Reflector	7
3	Icom IC-765 Modifications	7
3.1	W2ISB PBT mod	7
3.2	Modification for improved T/R Switching	8
3.3	Mod to prevent antenna switch unit failure	8
3.4	Improved monitor volume	8
3.5	Extended TX Mod	9
3.6	Better AM Audio	9
3.7	QRP mod	9
3.8	Selectable SSB Filters	10
3.9	Using the 250 Hz second IF CW filter in RTTY mode	12
3.10	New Version of the N6MZ Sidetone Tracking Modification	13
4	Common Problems	14
4.1	Antenna Tuner “Hunts” or “Chatters”	14
4.1.1	Empirical Technique	14
4.1.2	Alternate Technique	15
4.2	Problems covered in the Icom service FAQ.	15
4.3	VOX Oscillates	17
4.4	W8AEF’s Problems and Fixes	18
4.5	Carrier Oscillator Trimmer Adjustment Corrections	21
4.6	Icom 765 PLL Trimmer Repair — A Case History	22
5	Operating Hints	27
5.1	AM Operating Suggestions	27
5.1.1	Comments on the IC-765 on AM	28
5.2	PSK31: CW Receive and LSB Transmit	28
5.3	CW Keyer Speed	33

6	Microphones	33
6.1	Connection to an MC-60A Microphone	33
6.2	Using a computer headset	33
7	Change Log	35
7.1	V1.00, 2002.01.2	35
7.2	V1.01, 2002.01.30	35
7.3	V1.02, 2002.09.10	36

Copyright ©2002 Don Stalkowski.

The author and editor of, and contributors to this document provide NO WARRANTY; not even the implied warranty of MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE. This document may be reproduced and distributed as long as the above copyright notice and this paragraph are preserved on all complete or partial copies.

The home site for this document is: <http://www.execulink.com/~dstalk>

See Adam's (VA7OJ/AB4OJ) site (<http://www.qs1.net/ab4oj/>) for more IC-765 stuff.

I'd like to thank all those whose information I've used. Your contribution to Icom users is appreciated.

Finally, if you see something of your's here that you feel shouldn't be here, or that you haven't been credited for, or would like changed, or . . . , or if you see anything that contains errors or think something should be added or deleted, please contact me at dstalk@execulink.com.

1 Introduction

For an older rig, the IC-765 causes a lot controversy and passion. Opinions vary from bad to "you can have my 765 when you can pry it from dead cold hands! <:}" [George, W5YR]

The consensus seems to be that it's one of Icom's bests and that if the PBT (pass band tune) patent problems hadn't cropped up and Icom hadn't gone to cheaper filters, that it would have been close to the very best. Today it represents good value as a used transceiver.

This document is a collection of clippings from the Icom email reflector, information from various web sites, and other notes I've amassed on the IC-765.

1.1 Warnings

Although I've tried to collect the information in this document from reliable sources, there is absolutely no guarantee that any of it is correct. You are strongly encouraged to verify all information on your own. In particular, if modifying or repairing the transceiver, heed the following:

- Check as many sources as possible to verify the modification/fix.
- Understand the modification/fix. Know what it does, how it does it, and what circuit changes are required. Be sure that the modification/fix actually implements those changes.
- Be aware that even though a modification/fix may be acceptable for some radio, it may not be suitable for your's. Numerous production changes nor-

mally take place during the life of a radio and, in theory, every radio could be unique. Calvin [3] illustrates this fact.

- If you're not qualified to do it or don't completely understand the radio and the modification/fix don't touch it. Either use a competent repair facility or leave the radio alone.
- If you do discover an error in this document please inform the author(s) so that the information can be corrected.

2 General Information

2.1 Description

Features

- Automatic antenna tuner with tuning memory
- Direct Digital Synthesizer (DDS)
- Band stacking registers
- Built-in 500 Hz CW filters (9.0106 MHz and 455 kHz IFs)
- Built-in keyer, power supply, and CI-V
- CW pitch control
- RIT/ Δ TX controls
- 99 tunable memories

Specifications

Frequency Coverage: Tx: 1.8, 3.5, 7, 10, 14, 18, 21, 24, 28 MHz bands
Rx: 100 kHz – 30 MHz

Modes: USB, LSB, CW, RTTY, AM, FM

Dimensions: 424 x 150 x 390 mm
16.7 x 5.9 x 15.4 in.
17.5 kg; 38.6 lb.

Output Power: AM: 10–40 W, all other modes: 10-100 W

Major Options

- FL-53A (455 kHz) and FL-101 (9.0106 MHz) 250 Hz CW filters. Both 500 Hz and 250 Hz are selectable.
- FL-102 6 kHz AM filter.
- UT-36 voice synthesizer.
- UT-30 tone encoder.

2.2 Relation to the IC-761

[From: Adam Farson, VA7OJ/AB4OJ]

The IC-765 was actually a very different radio from the IC-761. These are the principal differences:

Synthesizer: 761 — PLL, very similar to IC-751A; 10 Hz resolution.
765 — DDS/PLL; 1 Hz resolution.

IF filtering: 761 — PBT and IF shift, selectable.
765 — IF shift only, bypassing 9 MHz filter.

SSB IF filters: 761 — FL-80/FL-44A (Icom's best SSB filter pair, also used in 751A).
765 — FL-30/FL-96 (wider, cheaper).

Internal autotuner: 761 — AT-150.
765 — Microprocessor-controlled memory tuner, no preset controls.

The IC-765 processor is much more advanced than that of the 761 and 751A. In the 765, the operating system is stored in EPROM (as opposed to RAM in the older radios). Only dynamic data is stored in RAM. There is also a data bus linking the main processor to the autotuner control processor.

One of the benefits of the newer control architecture in the IC-765 is the band-stacking registers.

The IC-761 is, in fact, pretty well a repackaged IC-751A with more filter selections, a standard (rather than optional) internal mains power supply and a built-in AT-150.

There are also considerable circuit differences on the MAIN (IF) board between the IC-761 and IC-765.

2.3 Filters

[From: Adam Farson, VA7OJ/AB4OJ]

The FL-80 is the preferred “standard” filter. The FL-80/FL-44A combination is used in the IC-751A and IC-761.

The FL-30 has a -6 dB bandwidth of 2.3 kHz. The FL-80 is 2.4 kHz wide at -6 dB, but has a considerably better shape factor than the FL-30 (1.6 vs. 1.8).

Replacement of the FL-96 455 kHz SSB filter with either an FL-44A or an Inrad 455/2.4 is worth considering, as a means of improving adjacent-channel selectivity.

[From: Don, VE3HUR]

I installed the FL-102 AM filter and did not notice any difference.

2.4 Power Supply

[From: Mahlon, K4OQ]

The internal power supply in the 765 is essentially a PS-35 in a slightly different case. This being the case, the DC power connectors between the supply and the rest of the transceiver are the same as any other ICOM-standard six-pin DC power connector, INCLUDING the two AC power lines (watch how you wire your connector, in other words).

The 765 will run off of 13.8 VDC just fine, assuming that you connect your external DC supply in lieu of the internal supply.

2.5 Trimmer Capacitors

Icom has stated that all IC-765’s were made with plastic trimmer capacitors [From: Bill, WA9MXQ], although the DDS LPL trimmer on some units is ceramic. However, Adam (VA7OJ/AB4OJ) thinks that later radios came with ceramic HPL VCO trimmers and recalls that his s/n 29xx IC-765 did.

2.6 Serial Numbers and Dates

The first Icom advertisements that I’ve found were in magazines in May 1989. The last major distributor’s advertisement was in March 1994. The highest serial number I’ve heard of is just over 5000.

From the serial numbers that have been posted in the Icom reflector, I’d guess that the distribution is about:

01xxx	1989–1990
02xxx	1990
03xxx	1991–1992
04xxx	1992–1994

2.7 Icom Email Reflector

There is a moderated Icom email discussion group. To subscribe to it visit <http://mailman.qth.net/mailman/listinfo/icom> or send an email with the subject "subscribe" to "icom-request@mailman.qth.net."

An archive of the group is at <http://mailman.qth.net/pipermail/icom/>. An even older archive is at <http://www.qth.net/archive/icom/icom.html>.

3 Icom IC-765 Modifications

Sources of this information:

These mods have appeared in many places including <http://www.mods.dk>, and in messages from Lee Wells, and Adam Farson (VA7OJ/AB4OJ), but the sources I first used were:

[Jean-F Tanguy, VE2KAD] and [Don, VE1AOE]

3.1 W2ISB PBT mod

This modification was originally designed by Gerd Henjes, W2ISB.

1. Cut (or lift) cathode end of D63
2. Add a 1N914 - solder anode end to anode of D64
3. Cut W31 (brown wire) and solder to cathode end of D63 and cathode end of new diode.

IF SHIFT button out = PBT, IF SHIFT button in = IF shift.

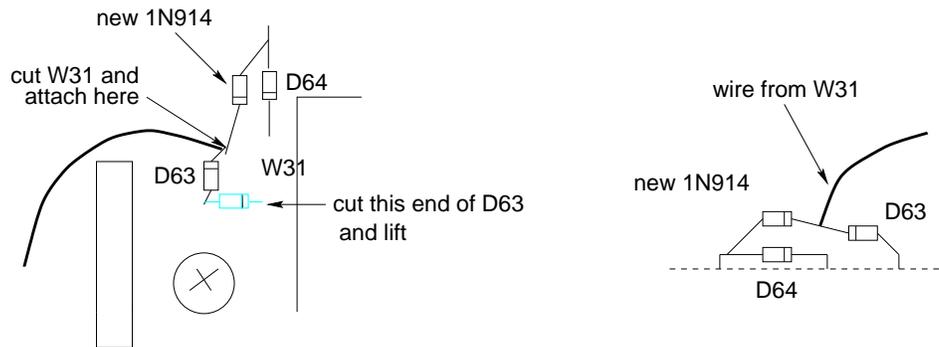


Figure 1: PBT modification top and side views.

3.2 Modification for improved T/R Switching

(prevents damage to D45, D46, D47, & D15 on RF Board.)

Parts Needed: 47K 1/8 watt resistor 150K 1/8 watt resistor 1SS53 diode Insulation for the resistor lead

1. Remove bottom cover
2. Remove screws from Main Unit and lift board
3. Remove R10 (39K) and R11 (39K) near IC-2
4. Install one end of new R11 (150K) to foil trace which connects to C13. Insulate remaining lead of R11 and solder it to Pin 3 of IC-2
5. Install new R10 (47K)
6. Solder D159 (1SS53) between Pins 3 and 13 of IC-2. Cathode side of diode (striped end) goes to Pin 3
7. Modification is complete. No adjustment is necessary. Reinstall the Main unit and Bottom cover.

3.3 Mod to prevent antenna switch unit failure

This modification is covered in the Icom service FAQ. The FAQ should be consulted for further information.

1. Remove top cover
2. Locate antenna switch unit at right rear of radio (at antenna jack).
3. Solder a 0.0047 uF, 500V ceramic capacitor to back side of pc board as shown. (Board removal is not necessary). The capacitor is effectively installed between ground and the junction of R1 and L1.
4. Reinstall top cover and check for proper transmitter operation. This modification prevents failure of R1, R2, D1 and L1.

3.4 Improved monitor volume

For radios with serial numbers below 2000.

1. Set radio for 8 MHz in LSB.
2. Adjust C226 for 1 to 1.2V at R201.
3. Verify that it goes to 3V at 7.9999 MHz.
4. Change R85(10K) on main unit to 4.7K.

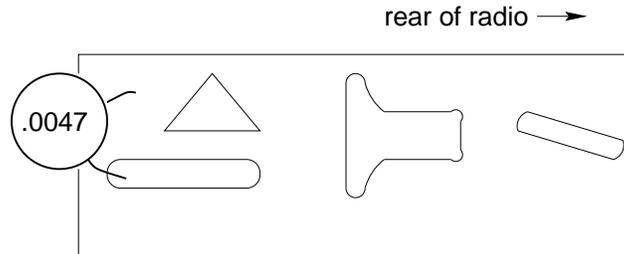


Figure 2: Rear of antenna switch circuit board.

3.5 Extended TX Mod

1. Remove top and bottom covers
2. From the bottom of the radio locate the matrix board which is next to the front panel.
3. Find diodes D50, D51, D52, D53, D54 and D55.
4. Cut one leg of D53
5. Assemble the radio and stay legal!

In addition, if you wish to use the antenna tuner, the following mod is required [From: Rick Robinson, K8DXN]:

1. Remove top cover.
2. Locate tuner control PCB. It is in the rear of the rig from the marker switch board.
3. Locate plug going to J103.
4. Find grey wire going to Pin 8 on J103 — named “TUNM” on circuit.
5. Remove grey wire — that all, done deal.

3.6 Better AM Audio

1. Replace AM rectifier diode with schottky for better audio.

3.7 QRP mod

With this circuit connected to the radio, the power output is adjustable between 0 and 100W. For best results, leave the RF power control at maximum and adjust for desired power using R2.

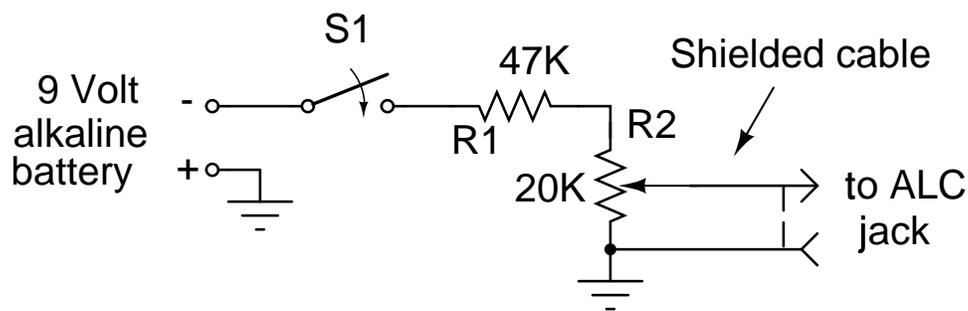


Figure 3: QRP adaptor for IC-765

S1 is used to turn off circuit when radio is not in use or QRP operation is not desired.

Radio Model:	R1 value	R2 value
IC-761, 765	47K	20K
IC-720(A), 735, 740, 745, 751(A), 275A/H	2M	1M
IC-725, 726, 728, 729, 736, 737(A)	220K	100K

06/01/94 CJR

For the IC-820H use the values for the IC-761, 765. The IC-781, IC-765 and the IC-820H all have the same ALC characteristics:

Control voltage: -4 to 0 volts
 Input impedance: More than 10 K ohms

3.8 Selectable SSB Filters

This mod was on my '765 when I purchased it. I don't think it's the best way to do it, but it works!

This unit has different SSB filters than a stock IC-765. An FL-70 (2.8 kHz) is used in place of the FL-30 (2.3 kHz) as the standard SSB filter. In addition, an FL-80 (2.4 kHz) is selectable via the "250 Hz" button on the front panel. The FL-80 is installed in the space allocated to the optional FL-101 250 Hz CW filter.

Filter	-6 dB	-60 dB
FL-30	2.3 kHz	4.14 kHz
FL-70	2.8 kHz	
FL-80	2.4 kHz	3.84 kHz

This modification is illustrated in figures 5 through 6.

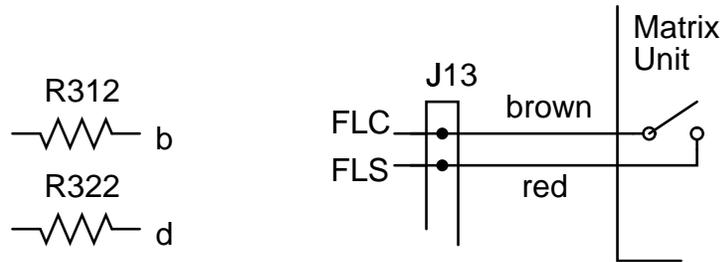


Figure 4: The Circuit Prior to Modification

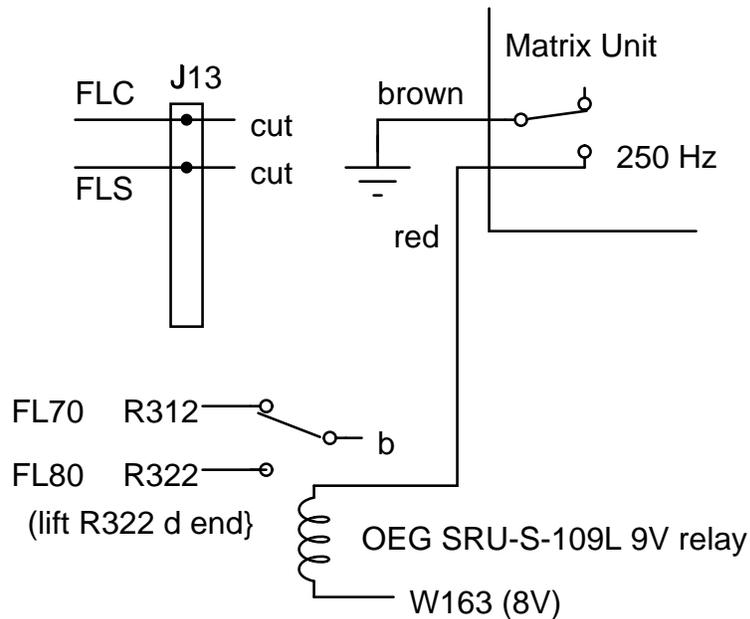


Figure 5: Circuit After Modification

The following steps perform the modification:

1. Cut the red (FLS) and brown (FLC) wires from J13.
2. Ground the brown wire (FLC).
3. Connect the red wire (FLS) to one end of the relay coil. Connect the other end of the relay coil to W163.
4. Cut W154.
5. Connect the end (“d”) of W154 nearest to the PCB edge, to the relay “common”.

6. Connect the other end (R312) of W154 to the relay NC connection.
7. Lift the end of R322, farthest from the filter, and connect it to the relay NO.

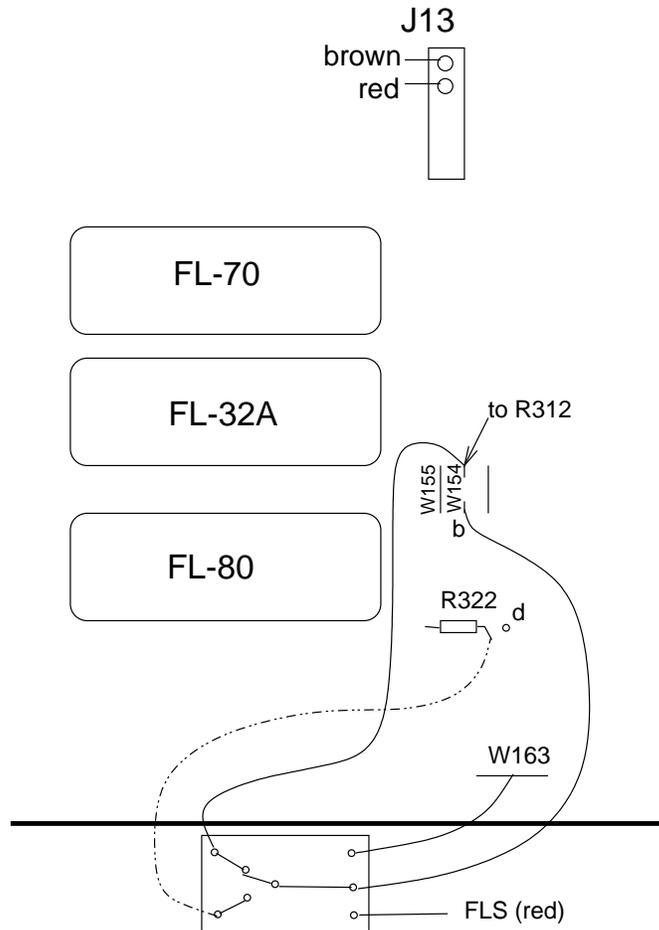


Figure 6: Pictorial of the Filter Modification

3.9 Using the 250 Hz second IF CW filter in RTTY mode

[From: Dave KD6TO]

This allows use of the 250 Hz second IF CW filter (FL-53A) in RTTY mode.

- Install the optional 250Hz filter according to the instructions (if not already installed).
- Remove the covers to gain access to the Main Unit PCB.
- Take a 1SS133 diode or equivalent and solder the positive side to the positive side of D42 (accessible at pin 15 of IC11) and the negative side to the negative side of D39.

- Re-assemble and test.

The CW 250Hz pushbutton will now select the 250Hz filter in both CW and RTTY modes.

3.10 New Version of the N6MZ Sidetone Tracking Modification

Michael Mraz, N6MZ, author of the May 1993 QST article titled “Add Tracking Sidetone to Your Icom IC-765 Transceiver” has suggested a new way of doing the modification:

I’d recommend doing the tracking sidetone another way. This mod is *much* simpler and actually uses the 765’s monitor mixer to beat the TX carrier oscillator against the RX BFO. The downsides are that the sidetone volume will vary a little, in proportion to the output power setting, and that you won’t hear the sidetone when you aren’t transmitting (i.e. you can’t do CW practice with the “VOX” button off).

This is what I did:

1. Remove Q16 on the Main board. This transistor cuts off the BFO during CW transmit.
2. Remove R77 on the Main board. This resistor couples the CW sidetone oscillator to the audio T/R switching circuit.

Now when you transmit, you should hear the actual tone resulting from the receive BFO beating with the transmit carrier oscillator. The volume of the audio sidetone will vary with the setting of the RF PWR control (more power = louder sidetone). If (and it’s a *big* if) all the mixer oscillators are aligned perfectly, when you tune the radio to match the sidetone frequency to the frequency of the received signal, you will be exactly zero-beat. My rig is accurate to within 10 Hz or so.

If you plan to work on the 765, you really should buy a copy of the service manual, it has all the two-color drawings that show the component locations on the boards. It also has the calibration procedure and theory of operation.

Floyd, K8AC, adds the following:

I installed the new mod and find that it works just as Mike describes. The variation in volume of the sidetone with the setting of the power control is of no consequence, since the sidetone volume is controlled by the monitor gain control (you must have the monitor ON to hear

the sidetone). While I haven't taken the time to measure the sidetone frequency against the received signal pitch, my ear says it's the same or extremely close.

If you don't already have a copy of the 765 service manual, you can get one from Icom. But — the manual they are currently selling is *not* a multicolor original, but a black and white copy. However, it's a very good copy, right down to the large fold out pages, and perfectly readable. Finding Q16 and R77 is certainly easier with the manual. If you plan to give this a try without the manual, you can find the two components just behind the shielded BFO enclosure on the main board. The BFO alignment information is found in the 765 Instruction Manual on page 47.

4 Common Problems

4.1 Antenna Tuner “Hunts” or “Chatters”

For either of these techniques the transceiver should be connected to a proper 50 Ω dummy load. Since the IC-765 apparently senses reflected power when tuning, it may be worthwhile to perform the final adjustments/checks with a “reasonable” power level, for example, 40 watts.

4.1.1 Empirical Technique

This is the fix most commonly presented.

The feedback circuit that controls the tuning motors becomes sensitive after a few months of aging. It requires a one time adjustment to correct.

1. Remove top cover and locate the antenna tuner board.
2. Locate R5 and R10 and set them to the center of their range.
3. Set radio as follows: Tuner on Frequency 14.100 MHz Mode RTTY
4. After transmit is engaged for 30 seconds,
5. Adjust each control (R5 and R10) so neither motor tunes while changing from SSB to RTTY and back to SSB.

Note: R5 (right) controls right motor and R10 (left) controls left motor.

6. Repeat this adjustment to verify proper operation and then check on all other bands.
7. Reinstall top cover and return to operation.

4.1.2 Alternate Technique

This is an alternate adjustment procedure that may be more satisfactory.

- Subject: The antenna tuner on some IC-765s “hunts” during transmit after the first tuning phase is complete. This may start after a few months of use.
- Information: The feedback circuit that controls the tuning motors may become sensitive after a few months of use.

1. Remove the top cover and locate the antenna tuner board.
2. Locate R5 and R10 and set them to the center of their range.
3. Set the following controls on the radio as indicated below:
Tuner — On Frequency — 7.1 MHz Mode — LSB
4. After transmit is engaged for 10 seconds (to allow the tuner circuits to tune and stabilize), and while still transmitting,
 - (a) Verify V-ref at R4 is between 4.6 and 5.3 VDC.
 - (b) Adjust R5 for a voltage that is one half of what was measured in step 5 \pm 0.1 VDC measured at R2.
 - (c) Adjust R10 for a voltage that is one half of what was measured in step 5 \pm 0.1 VDC measured at R7.
5. Verify proper tuner operation on all bands.
6. Reinstall the covers and return the radio to operation.

4.2 Problems covered in the Icom service FAQ.

The Icom service FAQ is copyright so I'm only going to list the problems covered in it. Refer to Icom

(<http://www.icomamerica.com/>) for their FAQ.

- Unit will not transmit or receive on all bands. Very low noise from speaker. Display and controls all seem to work properly.
- Dead spots in the bottom 250 kHz (or so) range of each band when radio is cold. Dead spots may eventually get smaller then disappear as radio warms up.
- No RX/TX when unit is first turned on, but will return if VFO knob is spun or if power is cycled on and off a few times.

- No RX/TX or distorted RX/TX on one or more bands. Distorted SSB audio sounds raspy and rough. Some bands may sound OK. Problem may be temperature related.
- Frequency unstable in SSB modes.
- Drastic change in audio frequency response between USB and LSB, i.e. USB audio has too much bass while LSB audio has too much treble. USB/LSB RX frequency response may be equalized, to a degree, by adjustment if the front panel IF Shift control. TX frequency response remains poor.
- No or very low RX sensitivity.
- Distorted RX on strong signals. BC band RX sensitivity may be low or marginal.
- Intermittent RX sensitivity. Problem seems mechanical. Banging on case or switching between RX & TX may temporarily restore sensitivity.
- RX disappears when outer shield of coax is connected to the antenna. Inspection reveals 6 volt DC at the center conductor of the antenna jack.
- PTT does not operate. When the SEND switch is flipped, the green RX LED stays lit and unit does not go in the transmit mode. Problem may be intermittent.
- No TX output in all modes. Problem is traced to no output at J8 on the RF unit.
- Distorted/raspy-sounding TX in SSB modes. Average power is low, even at higher mic gain levels. Turning on the speech processor seems to help a little. CW, RTTY and FM seems normal.
- No or low output on all bands with high Icc. Inspection reveals burned D1, L1, L2, R1, and/or R2 on the ANT SW unit.
- The power clicks off or flutters on and off when the TX power output is increased toward maximum. Inspection reveals that the internal power supply is unable to handle the current. Unit runs fine when the internal power supply is substituted with an external power supply.
- Tuner operates properly when a carrier is present, but drifts out of tune in SSB mode.
- Tuner “chatters” or makes a rattling sound while speaking into the microphone in SSB mode, mostly on upper bands.

- Tuner does not tune on any band. Inspection reveals that only one motor is turning.
- Intermittent display. S-meter may peg and RX/TX may disappear when the unit is in the failure mode.
- VFO tuning is erratic: Sometimes skips frequencies in a certain area of VFO knob travel. 10 Hz display digit “flutters” instead of changing incrementally when the VFO knob is turned slowly.
- Loud, high pitched squeal emanates from inside radio. May be intermittent.
- TX monitor gain seems low, even at maximum volume settings. Radio has good mic gain, and the transmitter works OK.
- A mechanical whine emanates from inside radio in TX only at certain power levels. Transmitter works OK.
- CI-V interface does not work. Unit will not communicate with computer.

4.3 VOX Oscillates

[From: John Bielefeld, K1JEB]

I have come up with the reason why my IC-765 VOX oscillates. The 8V power for the Mic Pre-amp comes from the Main Unit Board. But daisy chains through to and from other boards. This causes some transients to be induced in the 8V power line. The line is also made of a small gauge wire. The resistance on this line is high enough for these transients to be quite large enough to trip the VOX. Also if you listen to the transmitted signal via the internal monitor you can hear some of the digital noise generated.

The solution is:

1. Remove the 8V power pin 7 from connector J302 AF VR UNIT.
2. Remove the 8V power pin 3 from connector J103 NB SW UNIT.
3. Connect The 8V power pin (which came from pin 7 from connector J302 AF VR UNIT) to pin 3 to connector J103 NB SW UNIT. You may have to cut some tie wraps to do this. Just add some new tie wraps when you are done.

Ok, now the AF VR Unit has no 8V power. So we need to get this 8V power from the spare 8V power, pin 5 of J15 on the MAIN UNIT. I found some extra push in pins from an old VCR tape player. Add an extra push in crimp pin into pin 5 of the female connector for connector J15. Next run a wire (feeding through the tie wraps) to the AF VR UNIT. Find another push in crimp pin. Connect the

8V wire to this pin. Then push this pin into pin 7 of the male connector which plugs into J304 on the AF VR UNIT.

One item I did but not necessary is to use a thicker gauge wire for the ground return between the AF VR unit pin 8 J302 and the ground pin on the MAIN UNIT pin 1 J15.

I also ran the shielded audio cable from the mic pre-amp and the VOX input along the metal chassis and away from the noisy harness it was tie wrapped to. This helped some but not as much as the power cable change.

With this mod, I now have very, very clean audio from the mic pre-amp.

I would highly recommend this mod. It took me 2 hours to do.

4.4 W8AEF's Problems and Fixes

[From Paul M. Playford, W8AEF]

I have received several emails regarding my experiences with my IC-765 so here they are:

First, my '765 is s.n. 002313 purchase new about 1990.

After a couple weeks in the operating position I sensed that something was wrong — couldn't make any contacts. Nobody would answer my calls on 20 meters. Put the 303-401 back on line and no problems. After much checking I determined that FL30, the 9 MHz SSB filter had a very deep notch on one side of what was supposed to be the flat top, along with a sharp spike on one side of the pass band.¹

The net result was with my voice characteristics, the meters would wiggle but nothing came out on USB. Icom sent me a new filter but it had a deeper notch than the original so I installed Fox Tango ssb replacement filters in both IFs and the radio works great now.

I fell in love with it. Started to learn how to use some of the bells and whistles and (I think) work stations the old Heath stuff couldn't have. Then more troubles started.

1. Intermittent transmit — Cold solder joint on one end of the meter current shunt.
2. Receiver dead — 2 filter switching diodes shorted in the receiver.
3. Receiver dead — RF transistor in the receiver went open.

¹Adam, VA7OJ/AB4OJ comments: This is related to the whole sorry PBT patent-infringement tale. Earlier IC-765's (S/N < 3000) had up to 6 dB of SSB IF passband ripple, due to mis-termination of the IF filters. This was left behind when the circuit designers, working under a court deadline, hastily "yanked out" the IC-761 PBT circuitry. This ripple causes severe attenuation of highs in the recovered audio when PBT is cranked up. I understand that the problem was corrected for S/N > 3000. Note that in any event, the circuit changes involved in the PBT mod do not change the filter terminating impedances.

Checked with Icom and they sent me a copy of the factory update to the main unit to prevent future failure of these components. The update has already been installed in my radio and the diode is also installed correctly.

4. Intermittent transmit — Cold solder joint on receiver Q7 PTT transistor.
5. Radio dead — Open winding in T1 in the regulator unit. This is a small transformer that “kick starts” the power supply on turn on.
6. Computer interface not working. Replaced defective L4 in CT-17 Communication Interface-V.
7. Frequency readout jumps while tuning. Icom’s fix for this is to replace the optical encoder. It’s long out of warranty by now and I’m too cheap for that so I just repositioned the circuit board inside the encoder until the frequency readout didn’t jump.
8. Frequency changing — this one I haven’t found yet. It is intermittent and sounds like the IF SHIFT is wandering. Doesn’t happen often and when it does I power down the radio and it goes away. I just know it’s another cold solder joint but have not had any success locating it.

-5.0 volt supply is wandering.

The source of this -5.0 volt supply is IC7, located on the display unit. Removed the cover from IC7 and soldered three pins in it that had never been soldered. Several months later the display started flickering between dim and bright. I found 2 pins in this module that the solder had cracked (these were my soldered connections) because the pins are stiff and when you install the module on the display board the pins usually have to bend a little to fit the holes in the display board. When the pins don’t/won’t bend the solder gives. Be very careful when positioning these pins inside IC7 because the alignment is critical.

I replaced the three plastic trimmer capacitors in the BFO circuits (C42, C45 & C307) per paragraph 5 of the Most Common Service Questions for the Icom IC-765 I found on the ICOM web site. Symptom: Frequency unstable in SSB modes.

9. Replaced the three plastic trimmer capacitors in the Carrier Oscillators (C123, C125 & C128). Symptom: CW was transmitting about 2 KHz higher than receive. Made it a little <grin> difficult to make contacts.

Further: paragraph 4 of the above mentioned Most Common Service Questions suggest replacing C11, C20, C29 and C37 on the PLL unit. I did this as a preemptive strike before they gave me problems.

I have made several modifications to my ’765 (in addition to the repairs). The tracking sidetone that appeared in the May 1993 issue of QST is a

must do. I had the variable bandwidth tuning from the March 1991 issue of QST installed but removed it when my frequency changing intermittent arose. I will be re-installing the W2ISB PBT modification (it will allow both IF SHIFT and variable bandwidth) as the IF SHIFT is useless, but the PBT works very well. I have also installed PIN diodes in the receiver filter switching. This is what I call a preemptive strike — not sure if they improved the performance but a 50KW am station just went on the air about 5 miles from my QTH.

March 18, 1998

10. No transmit, receive OK. Transmit seems to produce about a 50 watt oscillation even in SSB and CW (not keyed).

Replace defective IC1, Q21, Q15, D46, D47, D45, Q14, Q8, C181 and C179. I think C179 shorted out first, causing the antenna relay to stick in the receive position even while transmitting. Screwing up the transmit impedance, caused the oscillation and blew the components. All defective components on RF UNIT. I think it would be well to replace all .1 uF capacitors on this board.

Spring 2000

11. No transmit, receive OK. Replace defective Q14 on the RF unit. Replacing this transistor is getting old. I checked the ratings on the device and it's operation in this application is well within it's ratings. Close inspection of the circuit reveals a possible path from the base thru C170, D45, C174, D47, C179 and RL1 on the RF UNIT, R211, L203, L204, C215, RL210 on the ANT SW UNIT, and on thru RL13 on the TUNER unit to the rear panel ANT connector. This is a real stretch to believe that could be a problem, but then I remembered that I have already replaced some of these components. So, just as a precaution I installed a pair of 1N4006 diodes in parallel, opposite polarity, across the antenna input terminals. Put the radio back on line and the first time I turned the antenna — WOW, what a racket! The loud buzz was only present while the antenna was turning. Pulled the antenna lead off the radio and measured 3–4 vac between the radio chassis and the coax. Checked the schematic on the T2X rotator and I see that the common between the two motor windings and one side of the brake solenoid are connected to the frame of the rotator. This point is also connected to the chassis of the rotator control box via the control cable. If I had a poor a.c. ground at the top of the tower (it's a crank up so I do) it is conceivable that while power was being applied to the motor and brake the ground potential at the top of the tower would actually float, due to IR losses

in the rotator control cable. This is what I found to be true and this floating ground potential is what is coming back down the coax inner conductor and blowing components in the RF UNIT. I plugged the controller into a 3 pin to 2 pin ac adapter (that lifts the ground) and the buzz went away. I have since corrected my grounding problem and it has been almost a year with no further failures in the rf unit. So, to those of us that lose components in the rf unit — check your ground between your rotator and radio.

12. After modifying my Henry 2K-3 for QSK I observed that each element was shortened during QSK operation. This originates in the 765 during full break in and was cured by adding a .047 uF ceramic capacitor across the normally closed contacts of the FULL BK-IN switch. This allows the VOX delay circuit to complete the element. I found the same modification in The Frankford Radio Club Newsletter — August, 1991 except they used a .022 uF Mylar Capacitor. I should read my notes and then I would not have to re-invent the wheel.

Now that it has been almost a year since the last failure I have more time to operate and reflect on why I have kept this radio. I am a DXer and contester and I feel this is the best radio available for this type of operating. I am particularly pleased that I have been able to keep my electronic trouble shooting skills sharp so I can repair my own equipment because, had I not found my own grounding problems, I would still be blowing components regardless of the radio I was using.

de Paul

– Some days you are the QSO, some days you are the QRM

W8AEF -*- ZF2TA (1992) -*- FO0PLA (1997) -*- 8Q7AA (1998) -*- XZ0A (2000)

4.5 Carrier Oscillator Trimmer Adjustment Corrections

[From: Mahlon Haunschild, K4OQ]

RTTY Shift Frequency adjustment (appears on page 6-10 of the IC-765 service manual):

All frequency measurements taken from the top of R484.

“WAS”

Adj. Conditions		Adjustment / Measurement
STEP 1:		
Freq. display:	14.10000 MHz	Adjust C123 for 9.01145 MHz
RTTY mode		
S2:	850 Hz	
S3:	NORMAL	
Transmitting		
STEP 2:		
S2:	170 Hz	Adjust C125 for 9.01077 MHz
STEP 3:		
S3:	REVERSE	Adjust C128 for 9.0106 MHz
STEP 4:		
FM MODE		Adjust L10 for 9.0100 MHz

“IS”

Adj. Conditions		Adjustment / Measurement
STEP 1:		
Freq. display:	14.10000 MHz	Adjust C123 for 9.01145 MHz
RTTY mode		
S2:	170 Hz	
S3:	REVERSE	
Transmitting		
STEP 2:		
S2:	850 Hz	Adjust C125 for 9.01077 MHz
STEP 3:		
S3:	NORMAL	Adjust C128 for 9.0106 MHz
STEP 4:		
FM MODE		Adjust L10 for 9.0100 MHz

4.6 Icom 765 PLL Trimmer Repair — A Case History

[Courtesy: Rich, KA8OKH, Updated 11-10-01]

See Rich's web page, (<http://home1.gte.net/web22jfw/>), for his original article.

I have had my Icom IC-765 HF transceiver for close to 7 years now. It has logged many (perhaps hundreds) of hours of use. This past spring, however, it began to develop some quirks. One day while it was receiving on 30 meters during a particularly busy contest weekend, I started noticing contest activity showing up on the band. The callsigns were recognized as leaders in the sport of contesting, and I found it odd that they would be active on this traditionally non-contest band. Another oddity — the signals were weak — weaker than I would expect from these high power stations. No matter... the contest ended that Sunday evening and things appeared to return to normal. A few weeks later, while operating on 40 meters CW, the receiver suddenly drifted 500 Hz up over the course of 5 seconds or so, and stayed there. A couple of days after that, everything received below 10 MHz would become garbled and unintelligible after 30–40 minutes of warmup.

At this point I decided that my trusty 765 was in need of some TLC. A few years ago I had printed out and read the 765 troubleshooting notes on the Icom web site (<http://www.icomamerica.com/support/troubleshooting/ic-765.html>), and I recalled something about raspy audio occurring after warmup, and that it sometimes affected certain frequency ranges. Sure enough, there it was — the dreaded plastic trimmer problem. Being a technician by trade, and not wanting to sacrifice my radio to the shipping gods for who knows how long, I decided to attack the problem myself. Here I'll describe for you how I got everything back into shape for just a few dollars and a few hours of time. The repair is not difficult. I feel that anyone with proper soldering technique and a decent digital voltmeter can do it. But if you feel squeamish about it, contact Icom Tech Support (<http://www.icomamerica.com>), and they will do the proper repairs for you.

What Happened?

What happens is this — the plastic trimmer capacitors in the PLL (phase lock loop) section of the radio are enclosed in a shielded can. This can also contains several coils that are covered with a wax to prevent (I presume) vibration. Also in the 765, the PLL board is located directly below the internal power supply. Now you would think that the heat would radiate up and away from the PLL unit, but enough heat reaches the board to slowly, over years, cause the wax to flow down into the trimmer caps. It then seems to eat away at the plastic dielectric of the trimmers, causing the HPL lock voltage(s) to drift out of acceptable range, which in turn causes all sorts of nasty things to occur. The raspy audio might just affect a certain range of frequencies, or several ranges, or all. In my case, it just affected everything below 10 MHz.

How do I Fix it?

Only one way — remove the plastic trimmers from the PLL board, and install ceramic replacement units. We'll go step by step, removing that nasty wax substance (or most of it anyway), and re-align the vco's according to the service

manual. While we're in there, we'll check out a few other things that may need attention. Time's wasting, so let's get started!

What You'll Need

- Soldering iron — 15–25 watt
- Solder wick — to remove solder from traces and shield cans
- Soldering gun — here we want something on the order of 100 watt
- 60/40 rosin core solder (I use Kester Rosin Core 44)
- #1 and #2 phillips screwdrivers
- Small pair of “nippy” cutters (wire cutters). Smaller the better
- Small “jewelers” type screwdrivers, preferably plastic handles, or similar adjustment tool
- Digital voltmeter

Of course you'll also need the replacement trimmer capacitors. The capacitors we'll be replacing are designated C11, C20, C29, and C37. C11 and C20 are 10pF (picofarad), while C29 and C37 are 7pF. Now... here's where I begin to deviate from the book a bit. First, let me say without equivocation — I have nothing against Icom service, or ordering replacement parts from them. However, in this situation I had the parts in hand to do this repair, and they work fine. But — if you feel that you should get these parts from Icom, by all means do so. Here are the Icom part numbers to ask for —

Icom part#

- 4610001130 — trimmers C11 & C20 (order two)
- 4610001000 — trimmers C29 & C37 (order two)

Now, having said that, you can also get suitable replacements from Digikey (www.digikey.com). They have to have leads spaced 4.5 mm apart, be ceramic, and of course be the proper capacitance. I found these Sprague GKG series ceramic units (<http://www.spraguegoodman.com/305/305p4.html>) to be more than adequate —

Digikey part#

- SG1029-ND — 3.5–10pF ceramic (white — Sprague part# GKG10024)

I used this 10pF unit for all 4 caps. Why? Well, C11 and C20 were 10pF anyway, but Icom recommends in their service notes that C29 be changed from 7pF to 12pF for ease of adjustment. C37 is(was) 7pF as well, so I figured why not try a 10 there as well? No worries — the 10pF works just fine for all 4 replacements.

Let's Start

Begin by laying your 765 on a CLEAN surface — a clean towel to keep from scratching your radio. So as not to cause any confusion here, *throughout this repair, keep the front of the radio facing you.* Remove the little door that covers the adjustments under the top cover, and set it aside. Remove the screws that hold down the top cover. Remove the top cover by gently lifting from the rear, then pulling back. Detach the internal speaker lead, noting the direction of the plug, and set the cover and screws aside. Now turn the radio over, and remove the bottom cover, and set it and the screws aside. Now flip the radio face up again. Ok, see that big black thing on the left side with cooling fins? That's your 765's power supply. Our bad caps are below it, so we have to get the power supply out of our way. It's held in by 4 screws — 2 of them go through the left side of the chassis, the other 2 go down on the right side of the power supply into two little chassis tabs. Remove these screws and unplug the two white interconnect cables going to the supply. Lift the power supply out, taking care to not damage the cooling fins, and set it and the 4 screws aside.

Now what you see on the left side of the radio is the PLL unit. It can be recognized by a few shield cans, one with 4 access holes in the top. We'll remove this board next. First, notice that there are a few cables that need to be disconnected. There is one grey coax that cannot be disconnected at the PLL board. It runs under the chassis to the RF unit. Turn the radio upside down. The RF unit is on the right side, under a shield cover. Remove all the screws holding the shield cover down and remove it. Notice the grey coax in front of the RF board that goes through a grounding clamp — this is the coax we need to disconnect. Remove the screw holding the grounding clamp. Trace the coax over to the RF board, and unplug it from the board. Pull the coax back through to the top of the radio. Turn the radio right side up again. Now remove the screws holding the PLL board down, and remove the board. Set the radio aside for now.

With the PLL board in front of you, again take note of the shield can with the 4 adjustment holes. Our 4 bad caps are under that cover (you can see them through the access holes), so this cover has to be removed. Using a soldering gun, apply heat to the corners of the shield cover, and use wick to remove the solder from these areas. It sometimes helps to gently pry on the corners with a small screwdriver while heating. Take your time, and don't apply too much force on anything.

Now flip the board over, and remove the lower shield from the area underneath the shield can. Using a solder gun, apply just enough heat to free each tab on the lower shield. Locate the mounting holes for the 4 caps, and desolder them using a 15–25 watt iron and solder wick. Now working from the top of the board, pull the old trimmers out (if they didn't fall out already). See all that tan gummy stuff inside the can? That's the wax that has caused our grief. Using a jewelers screwdriver, gently dig out the wax from the vicinity of the trimmer mounting

holes. If there are signs of wax that may later migrate down into the area of the caps later on, go ahead and gently remove it, taking care to not distort any coils or break any other components. If the wax is fairly solid, it sometimes helps to apply heat from a blowdryer while scraping.

After the areas have been cleaned, install the new trimmers in their proper positions and solder them in. Be sure to clip the leads flush with the board underneath so they don't touch the lower shield. At this point inspect all the traces underneath the shield can for possible cold joints and touch-up with a little solder as necessary. Icom recommends doing this before re-attaching the lower shield, so I suspect they have seen problems with solder joints here — so it's best to give it a good look-over.

Reassembly

Re-attach the lower shield to the underside of the PLL unit. Re-attach the top shield can cover (the one with 4 holes), taking care to orient the cover so you can see the trimmers through the adjustment holes, and solder the corners. Mount the PLL unit back into the chassis, taking care to not pinch any connecting cables. Re-attach all connectors. Re-route the grey coax to the RF unit, attaching the grounding clamp. Attach the coax to the jack on the RF unit. Replace RF unit shield cover.

With the radio right side up, connect the plugs to the power supply, but do not put the supply back in the radio yet. You can lean it up against the left side of the chassis for now. Plug the AC cord in, and attach some sort of antenna (dipole, piece of wire, whatever). Turn the radio on. Don't worry if you can't receive anything. You probably won't right now, as the new trimmers need to be adjusted.

Alignment

Remember — radio is right side up, facing you.

Now the Icom service manual says to use an oscilloscope to make these adjustments, but I obtained excellent results with a *good* digital voltmeter (DVM). Attach the dvm ground lead to the chassis. Attach the positive lead to resistor R6 on the PLL board. R6 can be found immediately to the left of the 4-holed shield can that we worked on — it's marked on the board. Next we'll make a series of adjustments to our new trimmers, working from the front trimmer (C11) to the back (C37).

- Set frequency to display 7.99999 MHz, and select LSB mode. Adjust C11 (the front adjustment hole) for a reading of 6.5 volts DC on the dvm.
- Set frequency to display 14.99999 MHz, LSB mode. Adjust C20 (2nd from front) for a reading of 6.5 volts DC on the dvm.

- Set frequency to display 21.99999 MHz, LSB mode. Adjust C29 (3rd hole back) for a reading of 6.5 volts DC on the dvm.
- Set frequency to display 29.99999 MHz, LSB mode. Adjust C37 (rear) for a reading of 6.5 volts DC on the dvm.
- Now check the voltage at the following 4 frequencies to ensure that it is more than 2 volts DC.

0.03000 LSB

8.00000 LSB

15.00000 LSB

22.00000 LSB

Together... Again

Re-install the power supply, taking care to not pinch any of the leads or damage the heat sink fins. Now would also be a good time to inspect the big white power supply plug for any signs of damage. Several 765 owners have had trouble with this plug, again due to heat. The plug will turn brownish in color, and become brittle. Contact Icom Service for a proper replacement.

Attach the top and bottom covers, speaker plug, and top access door. Enjoy!
Rich, KA8OKH

The author assumes no responsibility whatsoever for damages — absolutely nothing is expressed or implied here. Perform this repair at your own risk. If you feel this repair is beyond your ability, please contact Icom Service for repair/parts.

5 Operating Hints

5.1 AM Operating Suggestions

[From: Art Pightling, K3XF]

I have operated AM with many SSB/CW oriented multi-mode rigs as follows:

1. Set your microphone gain (in SSB) by speaking normally into your microphone as you observe alc action. (RF output is at max for this.) Start at zero mic gain and advance until you begin to see alc activity. Decrease mic gain just below this point so no alc activity is noted. Leave the mic gain at this point for the duration of your AM operation.
2. Turn on your compressor. Check to see that you do not exceed the alc range as you speak normally into the microphone. If you do, adjust your compressor so you don't.

3. Determine what your full output power is on CW.
4. Set your output with the RF power adjust to 20–25% of that amount. Leave it there for the duration of your AM operation.
5. Switch to AM. You should have very close to 95% AM modulation with this process and sound pretty good. Do some on the air audio checks to assure you are OK.
6. Turn on your amp and you will have a good signal without overdriving or splatter. Do some more on the air checks with the high power level. AM folks love this part — if you get disparaging remarks about the origin of your rig, tell them you are using this configuration until you finish your pair of 4-400s modulating a pair of 4-400s excited by your '765 ...

5.1.1 Comments on the IC-765 on AM

Adam Farson, VA7OJ/AB4OJ had this to say about using the IC-765 for AM:

The IC-765 is not really characterised for AM transmission. It fakes out AM by injecting an exalted carrier at the virtual-carrier point. In AM mode, the radio transmits only one sideband, whilst the newer DSP radios (IC-756, IC-756Pro/Pro II) generate a mathematically-perfect DSP AM (A3E) signal with the correct carrier/sideband amplitude relationships. I would not endorse the IC-765 as a high-end AM rig. The receiver is OK for SWL'ing, but lacks a synchronous demodulator.

5.2 PSK31: CW Receive and LSB Transmit

[From: George T. Baker, W5YR]

I have been asked by several fellow warblers to document the exact setup I use with my Icom IC-765 that allows me to receive PSK31 signals using the 500 Hz and 250 Hz filters. In the 765, and in many other rigs of its vintage, filter selection is tied to mode selection, and the narrow filters are available only in the CW Narrow or RTTY Narrow modes. Additionally the 765 allows 250 Hz filter use only in CW Narrow mode in which the 500 Hz filter is already engaged.

Peter (G3PLX) has made a strong case that narrow filters prior to the filtering operations within PSK31 have little beneficial effect on improving print in the face of strong adjacent signals. I agree completely and defend my use of narrow filters only on the basis of (1) they keep me from hearing a lot of QRM/QRN; (2) they possibly improve copy somewhat by keeping strong nearby stations from controlling the receiver AGC; and (3) I am accustomed to the sound of the receiver while receiving CW, my other favorite mode, and find it more natural to tune to a 700 Hz signal than to a 1000 Hz signal.

I had hoped to keep this note somewhat brief with only the procedural steps being described, but the length of the end product confirms that I failed.

A lot can be said on the theory of operation of the 765 which requires that certain of these steps be performed, but that is the subject of perhaps another note if enough folks are interested.

Setup for the PSK31 Program

1. Sample rate: whatever works for your system; 11025.0 works fine for me and provides a transmitted tone that is within much less than 0.1 Hertz of whatever PSK31 frequencies are selected.
2. Center Frequency: 700
3. Callsign
4. Inverted QPSK: checked, as we will be receiving on a lower-sideband mode when we select CW for receiving
5. PTT control: as appropriate
6. Narrow filter: personal preference — I like to use it so mine is checked.
7. On the main window, check AFC and NET. Tx and Rx frequencies will both be 700 Hz initially but will change with AFC and NET action.

Setup for the IC-765

1. Select VFO operation
2. Select SPLIT mode to receive on VFO-A and transmit on VFO-B
3. Set VFO-A to CW Narrow mode
4. Using VFO-A, tune in a PSK signal to a tone of 700 Hz to be centered in the waterfall display, much as you would tune a CW signal to that beatnote. Since the 765 tunes only in 10 Hz steps, you must allow PSK31 to do the final tuning within a 10 Hz range with the AFC function. Give the program a few seconds to AFC the signal to the center of the waterfall — note the new Rx Frequency and its offset from 700 Hz.

(I find it convenient to tune the 765 dial such that the offset is less than 10 Hz — more on this later: NOTE A)
5. With the PSK signal tuned in and centered in the waterfall, press ‘A=B’ and hold it until the function is completed (two beeps sound) in usual 765 fashion.

6. Press 'VFO A/B' to transfer control to VFO-B
7. Change the mode to LSB
8. KEY STEP: *increase* the dial reading by 0.7 (700 Hz). Example: you tune in the PSK31 station with VFO-A with the dial reading 14.071.53. When you have switched to LSB on VFO-B, change the dial to read 14.072.23, which is 700 Hz higher.

(This is the crucial step which causes the 765 to transmit your PSK31 signal on very nearly the same frequency as you are receiving — more on this later: NOTE B)
9. Return control to VFO-A with the 'VFO A/B' button
10. Continue, receiving in CW Narrow mode with VFO-A and transmitting in LSB mode with VFO-B.

WHEN YOU TRANSMIT, USING VFO-B IN LSB MODE, YOUR ACTUAL TRANSMITTED FREQUENCY WILL DIFFER SLIGHTLY (10 HZ OR LESS) FROM THAT OF YOUR CONTACT SINCE YOU CAN ONLY SET FREQUENCY IN THE 765 TO THE NEAREST 10 HZ. DON'T WORRY — ON AVERAGE YOU WILL BE OFF NO MORE THAN 5 HZ AND AFC AT THE OTHER END WILL SHORTLY HAVE YOU TUNED IN ON THE NOSE! THE NET AND AFC CAPABILITIES AT EACH END WILL KEEP THINGS TOGETHER.

Now, all that sounds complicated and long and tedious — it does because I almost told you how to build a clock when you asked for the time. Operationally, it is much simpler:

1. Tune in the PSK31 station with VFO-A
2. A=B and change to VFO-B
3. VFO-B to LSB and 0.7 higher dial reading
4. Back to VFO-A and carry on

That is the brief procedure that you do each time you change to a different frequency/station, but in return for those few seconds of button-pushing and knob-twisting, you get 500 Hz and/or 250 Hz selectivity.

Now, for some fine print:

Note A

PSK31 can “grab” a signal anywhere in the waterfall, up to 250 Hz away from center, and with a mouse click move it to the center and adjust the Rx Frequency and Tx Frequency to match. That is good and convenient. But, there are two possible “gotchas” here!

First, we have to be careful to ensure that our transmitted frequency (which will be the LSB dial frequency less 700 Hz \pm the AFC-controlled offset from 700 Hz) remains sufficiently within the transmitter LSB passband to output the power we desire. The problem here is that 700 Hz is down a bit on the SSB filter skirt and, on my rig, just barely puts out full power as compared with a 1000 Hz signal which is well within the filter passband and produces full power easily. Your mileage may vary as not all filters are the same. I did find that lowering the Tx Frequency to 600 Hz or below noticeably reduced the transmitter power output. In any event, since most folks seldom run over 50 watts output on PSK31 this small power reduction should not be a problem.

Second, the other side of this coin concerns the CW Narrow filters which are effectively centered on 700 Hz. If we use a Rx Frequency very far removed from 700 Hz, we run the risk of operating on or near the filter skirts with decreased output and possibly some slight phase distortion. My tests show that if Rx Frequency remains within about \pm 100 Hz of 700 Hz, the received signal remains well within the 765’s 250 Hz filter passband.

In summary of this point, you can operate with a Rx Frequency from about 600 Hz to about 800 Hz with no problem from the 765 receive filters. You can transmit at any reasonable frequency *above* 700 Hz and again no problem. But, if Tx Frequency is much below 700 Hz your transmitted signal power will be decreased.

Note B

The procedure above specifies that 0.7 is to be added to the received signal frequency when adjusting VFO-B in LSB mode.

THIS IS THE CORRECT NUMBER *ONLY* IF THE 765 BFO FREQUENCIES ARE CORRECTLY ADJUSTED.

If your 765 has not been recently aligned, a simple test will enable you to correct for any mis-alignment and still use the procedure.

In Step 10 above when you have returned to VFO-A, verify that the PSK31 signal is still centered in the waterfall and note the RX Frequency reading in the window. In particular, note the offset from 700 Hz. Now, press ‘VFO A/B’ to return to LSB mode. If your 765 is correctly aligned, you will be within a few Hertz of the same Rx Frequency and within a few seconds, the phase scope will be centered. Note the total frequency difference between Rx Frequency with VFO-A and with VFO-B after the AFC has settled down. That is the total frequency difference with which your signal will be received at the other end and is the amount that the other station’s AFC will adjust for your signal.

If the required frequency change is over 10 Hz, then your BFO frequencies are off. However, this is easily compensated for without realignment of the 765. With VFO-B simply adjust the dial reading slowly up or down in 10 Hz steps until you find the dial reading in LSB mode that gives the *smallest* Rx Frequency difference between using VFO-A and VFO-B. That will also be the dial reading that comes closest to centering the phase scope and gives you good print. When you have the right value, the signal should sound exactly the same in either receive mode, except for the added noise, etc. in the LSB mode. Subtract that dial reading from the VFO-A dial reading, or vice versa, and that is the number that you add to the VFO-A dial reading in Step 8, instead of 0.7.

An example: VFO-A dial is 14.071.53. You find that you have to set VFO-B dial to 14.072.24 instead of the 14.072.23 we used in the example in Step 8. The difference is $14.072.24 - 14.071.53 = 0.71$. So, the frequency value for your radio to add to the VFO-A dial reading will be 0.71 instead of the ideal 0.7. It works the other way as well. Suppose that your dial reading is 14.072.22. Subtracting this from 14.071.53 gives 0.69 for your number. In both cases, one of the BFO frequencies is off by 10 Hz one way or the other.

This change from 0.7 makes no difference in system performance — you are merely correcting for a small discrepancy in 765 alignment. However, if the correction is more than a few tens of Hertz, you probably need to realign the BFO frequencies.

With the proper dial increment value in place, you can switch between VFO-A and VFO-B and except for the few seconds it may take the AFC to make its correction, you should get perfect copy while receiving in either mode. Again, on average, you will almost always be within 5 Hz of correct, centered tuning and that range will provide good print throughout.

Should your rig drift about, you might find that you need to change the actual frequency value you use as the “adder” but mine has remained very constant at 0.7 since I last realigned it a few weeks ago. I should also mention that my 765 stays on 24/7/365 as a precaution against drift and in connection with some other activities. In any event, each time you set up for another station, you will immediately find out if your adder is correct, and if not what the correct one should be. Just use whatever value gives approximately the same Rx Frequency values with CW Receive and LSB Receive.

As a final disclaimer, please note that most if not all micro-processor-controlled Icom rigs prior to the 765 change the dial frequency reading by a fixed amount when the mode is changed. I know that was true up through the 761. Obviously, the procedure given above would have to be altered to take that dial reading change into account. Since I do not have access to any other Icom rig, perhaps someone else can pioneer one of the earlier Icom’s for us.

I apologize for the length of this note, but I felt that more 765 owners would feel confident to try this operating style if I provided a little more than just a bare-bones “do this and then do that” procedure. I find that the few seconds required

to set up for a new station are well invested in return for the capabilities provided by the narrow filters.

Please direct any questions to me privately unless you feel that others might share your concern and would be interested in the answers. I especially invite users of other makes of rigs to see how this procedure, appropriately modified, works with their systems.

5.3 CW Keyer Speed

The internal keyer can be varied between 5 and 11 wpm (slow setting) and 10 and 48 wpm (fast) as shown in figure 7.

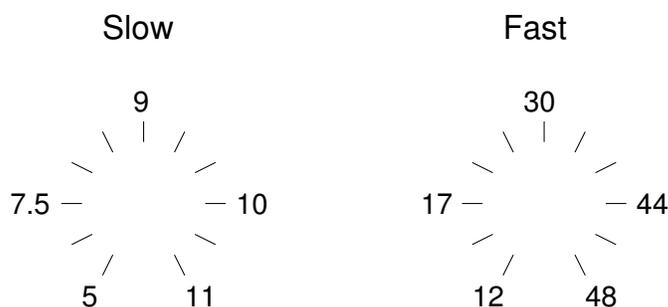


Figure 7: CW Keyer Speed

6 Microphones

6.1 Connection to an MC-60A Microphone

A Kenwood MC-60A may be used on an IC-765 if the existing cable is rewired or a new cable is made. The pinouts for the MC-60A and the IC-765 are shown in Figure 8.

Icom uses a single wire for Up/Down while Kenwood uses 2 wires. See Figure 9 for the Icom scheme.

The wiring for a new cable is shown in Figure 10.


I wasn't pleased with the audio quality from this combination.

6.2 Using a computer headset

Rick Meilstrup, OZ5RM describes how to use a computer headset with an IC-765:

A cheap headset (\$12-15), like the kind used with a computer, makes an excellent, light-weight replacement for a separate mike and speaker. In order to connect it to our IC-765 we have to make an adaptor. I used an empty film canister. Two small sockets are fitted on the can's

Kenwood MC-60A Wiring

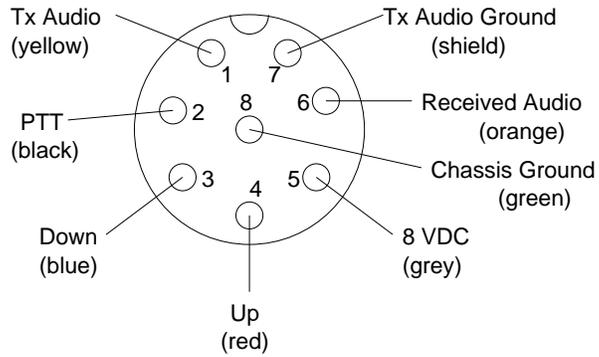

(colours are those used in my oem MC-60A cable)

Icom IC-765 Microphone Wiring

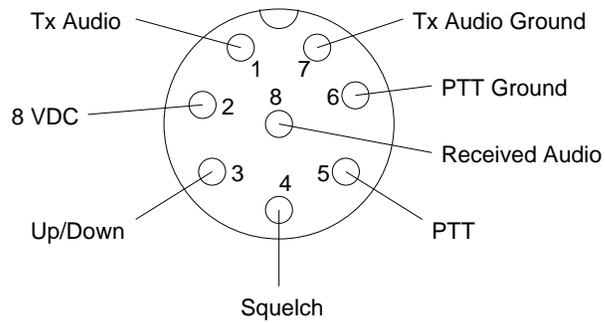


Figure 8: Microphone connectors. (Chassis connector as viewed from outside).

Icom Up/Down Wiring


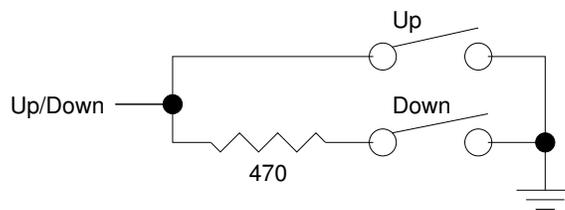


Figure 9: Icom Up/Down Wiring

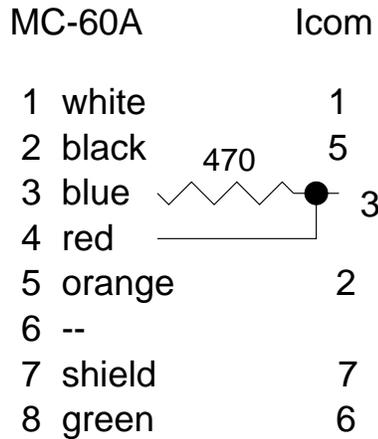

(colours are those used in my cable)

Figure 10: MC-60A cable for use with Icom IC-765.

lid, and a suitable hole is made in the bottom of the canister. An Icom 8 pin mike plug is fitted with a short length of shielded multicore cable and the other end of the cable is passed through the hole, then soldered to the two sockets, one for the mike, and one for the headphones. In order to have the sound appear in both sides of the 'phones I short-circuited the two stereo pins on this particular socket. There is no provision for PTT. Instead, I use VOX and adjust various controls on the 765. The audio quality is on par with my SM6 mike, so say my friends.

On my own adapter I added another jack for a separate push button PTT switch (from an old computer game). The microphone is connected to pins 1 and 7, the headphones (series or parallel, depending on impedance) to pins 8 and 6, and PTT to pins 5 and 6. Inside the IC-765 pin 1 is connected, via 1820 ohms of resistors, to +8V and this nicely powers the electret element.

7 Change Log

7.1 V1.00, 2002.01.2

- - initial release

7.2 V1.01, 2002.01.30

- - new high serial number
- - updated Icom email reflector info

- - updated antenna tuner adjustments

7.3 V1.02, 2002.09.10

- - KD6TO's filter mod
- - new sidetone mod
- - html version no longer supported

References

- [1] Exploring the synthesizer in a commercial mf/hf transceiver. In Paul Danzer N1II, editor, *The ARRL Handbook for Radio Amateurs*, chapter 14, pages 14.49–14.52. The American Radio Relay League, Inc., 75th edition, 1998.
- [2] Mark J. Wilson AA2Z. Icom IC-765 160- to 10-meter transceiver. *QST*, pages 52–55, December 1990.
- [3] Duane A. Calvin AC5AA. Icom IC-765 mods revisited. *QST*, September 1996. See Straw Dec 1995.
- [4] Rich Guski KC2MK. Variable-bandwidth tuning for the Icom IC-765 transceiver. In *Hints & Kinks 13th Edition May 1992*, pages 1–17–1–18.
- [5] Rich Guski KC2MK. Variable bandwidth tuning for the Icom IC-765. *QST*, 1991.
- [6] Dean Straw N6BV. Modifying the Icom IC-765 for better sounding audio and agc. *QST*, pages 78–79, December 1995. See Technical Correspondence Sep 1996.
- [7] Michael A. Mraz N6MZ. Add tracking sidetone to your Icom IC-765 transceiver. *QST*, pages 39–42, May 1993.
- [8] Michael Cobuccio WA1EYP. The Icom IC-765. *73 Amateur Radio*, pages 22,25, February 1990.